



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

## COMPUTER STRUCTURE AND ORGANIZATION

### Assignment 1

---

**Prepared by: Karim Taha**

**number:1211155**

**Instructor: Dr Jamal Seyam**

**Assistant:Eng Borhan Adain**

**Section: 1**

**Date:5/14/2024**

## Table of Contents

<b>Question one</b> .....	6
<b>Micro_control</b> .....	6
<b>T (time sequence)</b> .....	7
<b>Register</b> .....	8
<b>Reg_8bit</b> .....	8
<b>reg_10bit</b> .....	9
<b>PC</b> .....	9
<b>IR</b> .....	10
<b>Memory</b> .....	11
<b>Decoder3x8</b> .....	13
<b>decoder2x4</b> .....	13
<b>Block Diagrams</b> .....	14
<b>T with combntional circuit</b> .....	15
<b>Test for the system</b> .....	16
<b>X3</b> .....	16
.....	16
.....	16
<b>X4</b> .....	17
<b>microcomputer</b> .....	19
<b>Question two</b> .....	21
<b>arithmetic circuit</b> .....	21
<b>Logic circuit</b> .....	22
<b>ALU</b> .....	23
<b>state controller</b> .....	24
<b>Hardware state</b> .....	25
<b>ALU with state controller</b> .....	26
<b>ROM8X14</b> .....	27
<b>CAR</b> .....	28
<b>Hardwar control with ALU</b> .....	29
<b>Blocks digrams</b> .....	30

**COMMON use circuit .....31**

## Table of figures

Figure 1: micro control code .....	6
Figure 2: microcontrol waveform .....	6
Figure 3: T wave form .....	7
Figure 4: one-bit register.....	8
Figure 5: one bit registeg wave form .....	8
Figure 6: 8 bit register .....	8
Figure 7: 10-bit register.....	9
Figure 8: PC counter code .....	9
Figure 9: PC counter wave form .....	9
Figure 10: IR code .....	10
Figure 11: IR wave form .....	10
Figure 12: memory code part1 .....	11
Figure 13: Memory code part 2 .....	11
Figure 14: Read wave .....	12
Figure 15: write memory.....	12
Figure 16: decoder3x8 waveform .....	13
Figure 17: decoder3x8.....	13
Figure 18: deocder2x4 code .....	13
Figure 19: decoder 2x4 waveform .....	13
Figure 20: combntional circuit block.....	14
Figure 21: memory block.....	14
Figure 22: T block .....	14
Figure 23: PC block .....	14
Figure 24: MAR block.....	14
Figure 25: IR block .....	14
Figure 26: R block.....	14
Figure 27: MBR block .....	14
Figure 28: A block.....	14
Figure 29: control unit with IR .....	15
Figure 30: control unit with IR wave form .....	15
Figure 31: X3 waveform .....	16
Figure 32: X3 test .....	16
Figure 33: X4 test .....	17
Figure 34: x4 wave.....	17
Figure 35: X8 tets .....	18
Figure 36: x8 wav.....	18
Figure 37: microcomputer block diagram .....	19
Figure 38: microcomputer block diagram waveform .....	20
Figure 39: arithmetiv circuit cod .....	21
Figure 40: arithmetic circuit waveform .....	21
Figure 41; arithmetic circuit Truth table.....	21
Figure 42: Logic circuit cod.....	22
Figure 43: logic circuit waveform .....	22

Figure 44:logic circuit Truth table .....	22
Figure 45:ALU code .....	23
Figure 46:ALU wave form .....	23
Figure 47:state control waveform .....	24
Figure 48:state_ controller .....	24
Figure 49:Moore machine code.....	24
Figure 50:hardware state .....	25
Figure 51 state with output .....	25
Figure 52hardware state wave .....	25
Figure 53:ALU with state control block .....	26
Figure 54 alu with state wave form .....	26
Figure 55:ROM8X14 code .....	27
Figure 56:ROM8X14 waveform .....	27
Figure 57:CAR code.....	28
Figure 58:hardwire control implmen.....	28
Figure 60:hardware control with alu .....	29
Figure 59:Question2 output .....	29
Figure 61:E.....	30
Figure 62:ALU.....	30
Figure 63:control unit .....	30
Figure 64:A&B .....	31
Figure 65:Mux2x1 .....	31
Figure 66MUX2X1 block.....	31
Figure 67:Decode 2X4 block .....	31
Figure 68:decoder 2x4 .....	32
Figure 69:MUX4x1 .....	32
Figure 70:Dflipflop.....	32
Figure 71:Decoder3x8 BLOCK.....	32
Figure 72:Decoder 3X8 .....	33
Figure 73:Tflipflop .....	33

## Question one

### Micro\_control

```
1 module micro_control(output x8,x7,x6,x5,x4,x3,x2,x1 , input [3:0]q,input [7:0] t) ;
2
3 wire [8:0]a;
4 and g1(a[0],q[2],t[3]);
5 and g2(a[1],q[3],t[3]);
6 or o1(x1,t[0],a[0],a[1]); //x1=t0+q2.t3+q3t3
7 and g3(x2,q[3],t[5]); //x2=q3.t5
8
9 and g4(a[3],q[2],t[4]);
10 and g5(a[4],q[3],t[4]);
11 or xo2(x3,t[1],a[3],a[4]); //x3=t1+q2.t4+q3t4
12
13 and xa4(a[5],q[3],t[6]);
14 or xo4(x4,x3,a[5]); // x4 =x3+q3.t6
15
16 and xa5(a[6],q[2],t[5]),
17 xa51(a[7],q[3],t[7]);
18 or xo5(x5,a[6],a[7]); //x5 =q2.t5+q3.t7
19
20 and xa6(x6,q[1],t[3]); //x6=q1.t3
21
22 or xo7(x7,x5,x6); //x7=x5+x6
23
24 buf (x8,t[2]); //x8=t2
25 endmodule
```

Figure 1:micro control code

 


Figure 2:microcontrol waveform

## T (time sequence)

```
1 module T_reg(output [2:0] Q ,input count,clk,reset);
2   //T_reg id 3-bit counter that count when count = 1 and remian the same if count = 0 , Reset when reset = 1 ;
3   wire q01 ;
4   and A0(q01,Q[0],Q[1]);
5   T_FF t0(Q[0],count,clk,reset),
6       t1(Q[1],Q[0],clk,reset),
7       t2(Q[2],q01,clk,reset);
8
9 endmodule
```

 


Figure 3:T wave form

The counter will count from (000-111) and reset when reset =1 the and the counter work at the positive edge of the clock T(output of counter) will enter the 3x8 decoder 3-bit input When T=000 the decoder will make t0 active

## Register

```
1 module one_bit_reg(output Q , input data,select,clk,reset );
2
3 wire muxout;
4 mux2x1 (muxout,Q,data,select);
5 D_FF(Q,muxout,clk,reset);
6
7 endmodule
```

Figure 4:one-bit register

To create the register, a mux 2x1 and a D flip-flop were used. The output Q from the D flip-flop and the load data were fed into the mux 2x1. The output of the mux was then connected to the input of the D flip-flop. In this manner, a one-bit register was constructed. To create a 10-bit register or an 8-bit register, 10 or 8 such circuits from this model would be needed.

 


Figure 5:one bit registeg wave form

## Reg\_8bit

```
1 module reg_8_bit (output [7:0] Q ,input [7:0] data ,input select,clk,reset) ;
2
3
4 one_bit_reg r0(Q[0],data[0],select,clk,reset),
5               r1(Q[1],data[1],select,clk,reset),
6               r2(Q[2],data[2],select,clk,reset),
7               r3(Q[3],data[3],select,clk,reset),
8               r4(Q[4],data[4],select,clk,reset),
9               r5(Q[5],data[5],select,clk,reset),
10              r6(Q[6],data[6],select,clk,reset),
11              r7(Q[7],data[7],select,clk,reset);
12
13
14
15 endmodule
```

Figure 6: 8 bit register



## reg\_10bit

```

1  module reg_10_bit (output [9:0] Q ,input [9:0] data ,input select,clk,reset) ;
2
3
4
5
6
7
8  |
9  one_bit_reg r0(Q[0],data[0],select,clk,reset),
10 r1(Q[1],data[1],select,clk,reset),
11 r2(Q[2],data[2],select,clk,reset),
12 r3(Q[3],data[3],select,clk,reset),
13 r4(Q[4],data[4],select,clk,reset),
14 r5(Q[5],data[5],select,clk,reset),
15 r6(Q[6],data[6],select,clk,reset),
16 r7(Q[7],data[7],select,clk,reset),
17 r8(Q[8],data[8],select,clk,reset),
18 r9(Q[9],data[9],select,clk,reset);
19
20
21 endmodule

```

Figure 7: 10-bit register

## PC

```

1  module PC (output reg [7:0] address,input count, reset);
2
3
4  always @(posedge count or posedge reset)
5  begin
6      if (reset)
7          address <= 4'h00; // Reset to 0x00
8      else if (count)
9          if(address < 8 )
10             address <= address + 1'b1; // Increment on count
11         else
12             address <= 0 ;
13     end
14
15
16 endmodule

```

Figure 8:PC counter code

 


Figure 9:PC counter wave form

Pc counter will contain the address for next instruction to be fetched and decoded

## IR

```

1  module reg_10_bit (output [1:0]opcode ,output [7:0] Q ,input [9:0] data ,input select,clk,reset) ;
2
3  one_bit_reg r0(Q[0],data[0],select,clk,reset),
4      r1(Q[1],data[1],select,clk,reset),
5      r2(Q[2],data[2],select,clk,reset),
6      r3(Q[3],data[3],select,clk,reset),
7      r4(Q[4],data[4],select,clk,reset),
8      r5(Q[5],data[5],select,clk,reset),
9      r6(Q[6],data[6],select,clk,reset),
10     r7(Q[7],data[7],select,clk,reset),
11     r8(opcode[0],data[8],select,clk,reset),
12     r9(opcode[1],data[9],select,clk,reset);
13
14
15  endmodule

```

Figure 10:IR code

 


Figure 11:IR wave form

The IR will divide the instruction to opcode that will go to the combinational circuit and the rest of the instruction will go to the MAR

# Memory

```

1 module RW_Memory16X14_final (output reg [9:0]data_out,input [9:0] data_in , input [2:0] address , input read,write,clk);
2 reg [9:0] Mem [15:0];
3
4 generate
5     integer i;
6     initial begin
7         for (i = 0; i < 5; i = i + 1) begin
8             case (i)
9                 0: Mem[i] = 10'b1100001011;
10                1: Mem[i] = 10'b1000001011;
11                2: Mem[i] = 10'b0110011111;
12                3: Mem[i] = 10'b1110011111;
13                4: Mem[i] = 10'b0100010001;
14                5: Mem[i] = 10'b1000001101; // LDI 10 , Mem[13] -> MBR -> A = 0x6E
15                6: Mem[i] = 10'b1100001110; // LDA 11 , Mem[Mem[14]] -> MBR -> A = 0x88
16                7: Mem[i] = 10'b0100001011;
17                8: Mem[i] = 10'b0100001010;
18                9: Mem[i] = 10'b0100001010;
19                10: Mem[i] = 10'b0100001011;
20                11: Mem[i] = 10'b0000001100;
21                12: Mem[i] = 10'b0001110111;
22                13: Mem[i] = 10'b0001101110;
23                14: Mem[i] = 10'b0000001111;
24                15: Mem[i] = 10'b0010001000;
25            endcase
26        end
27    end
28 endgenerate
29
30 always @(posedge clk)begin
31     if (write)
32         Mem[address]<= data_in;
33     else if (read)
34         data_out <= Mem[address];
35     end
36 endmodule

```

Figure 12:memory code part1

```

22         12:Mem[i] = 10'b0001110111;
23         13:Mem[i] = 10'b0001101110;
24         14:Mem[i] = 10'b0000001111;
25         15:Mem[i] = 10'b0010001000;
26
27         // Add more initializations for other memory locations if needed
28         default: Mem[i] = 10'b0000000000; // Default initialization to 0
29     endcase
30 end
31 end
32 endgenerate
33 always @(posedge clk)begin
34     if (write)
35         Mem[address]<= data_in;
36     else if (read)
37         data_out <= Mem[address];
38     end
39 endmodule
40

```

Figure 13:Memory code part 2

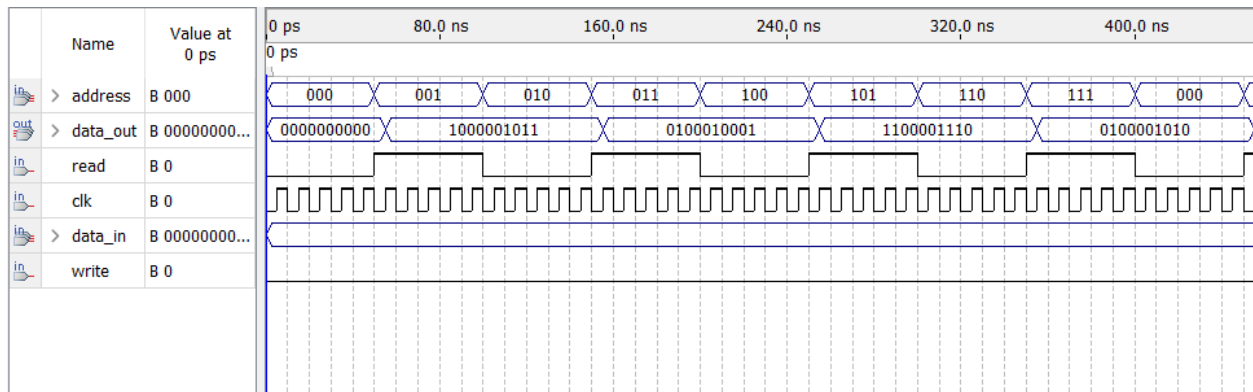


Figure 14:Read wave

At address 011 that means when Memory [3] the data will be 0100010001 so the memory reads the data from the memory with address 3 and the address will be getin from the mar

 


Figure 15:write memory

At address 001, the initial data in memory was 100001011. The new data to be written (data in) is 1101001110. After performing the write operation at address 001, the data at this address will be 1101001110. A read operation at the same address will now show this new data. The difference between the initial and the new data can be deduced by comparing figures 14 and 15 for the same address."

## Decoder3x8

```

1 module decoder3x8(input[2:0] in,output reg[7:0] out);
2
3   initial out = 8'b00000000;
4   always @(in )
5   begin
6     case (in)
7       3'b000: out=8'b00000001;
8       3'b001: out=8'b00000010;
9       3'b010: out=8'b00000100;
10      3'b011: out=8'b00001000;
11      3'b100: out=8'b00010000;
12      3'b101: out=8'b00100000;
13      3'b110: out=8'b01000000;
14      3'b111: out=8'b10000000;
15    endcase
16  end
17 end
18
19 endmodule

```

Figure 17:decoder3x8

 


Figure 16:decoder3x8 waveform

## decoder2x4

```

1 module decoder2x4(input[1:0] in,output reg[3:0] out);
2
3   initial out = 4'b0000;
4   always @(in )
5   begin
6     case (in)
7       2'b00: out=4'b0001;
8       2'b01: out=4'b0010;
9       2'b10: out=4'b0100;
10      2'b11: out=4'b1000;
11    endcase
12  end
13 end
14
15 endmodule

```

Figure 18:deocder2x4 code

 


Figure 19:decoder 2x4 waveform

Block Diagrams

 


Figure 20:combntional circuit block

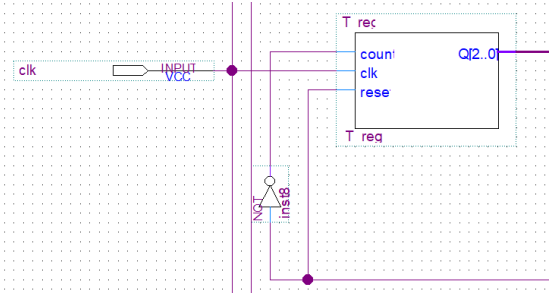


Figure 22: T block

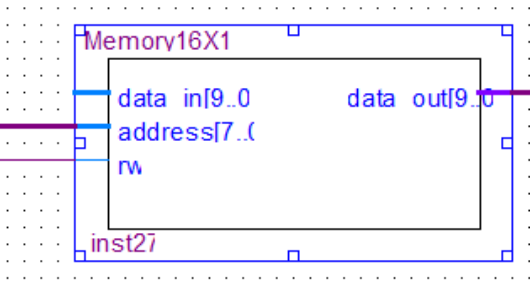


Figure 21:memory block

 


Figure 23:PC block

 


Figure 25:IR block

 


Figure 24:MAR block

 


Figure 27:MBR block

 


Figure 26: R block

 


Figure 28: A block

## T with combntional circuit

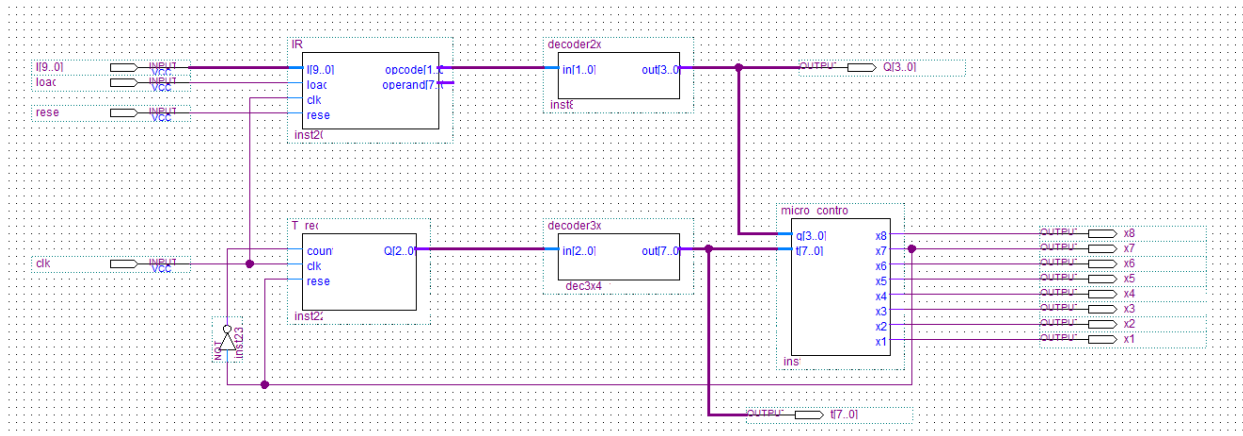


Figure 29: control unit with IR

 


Figure 30: control unit with IR wave form

[I] is the instruction it is a 10-bit instruction when the instruction enters the IR the IR will divide it to the opcode and address the opcode will go 2x4 decoder to determine the operation of the combinational circuit while the address will go to the MAR

If opcode equals 11 (LDA) the T will work for 7 state sequence(t0-t7)

, if opcode equals 10 (LDI) the T will work five state sequence (t0-t5)

Test for the system

X3

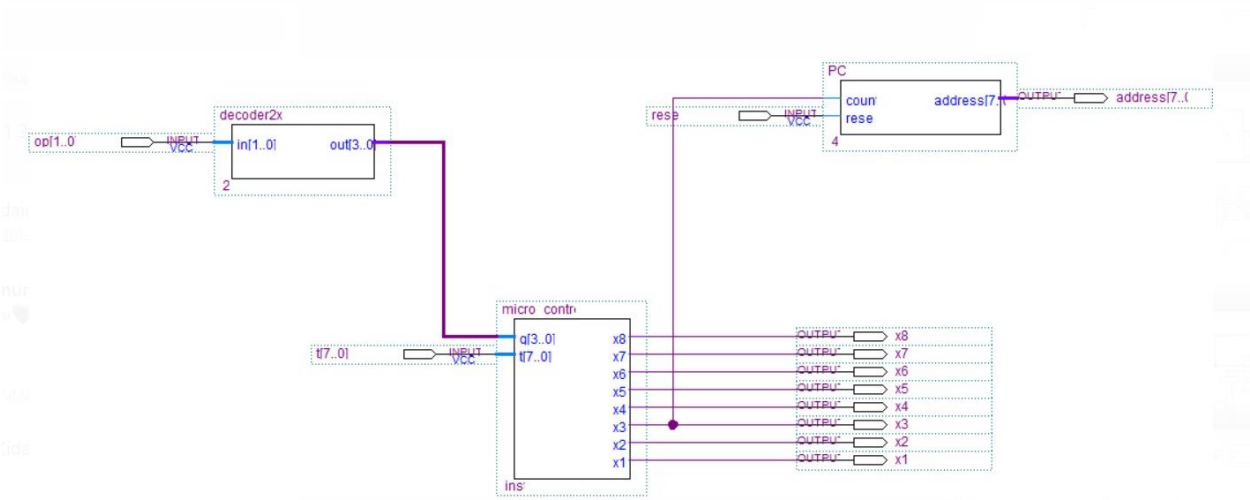


Figure 32:X3 test

 


Figure 31:X3 waveform



## X4

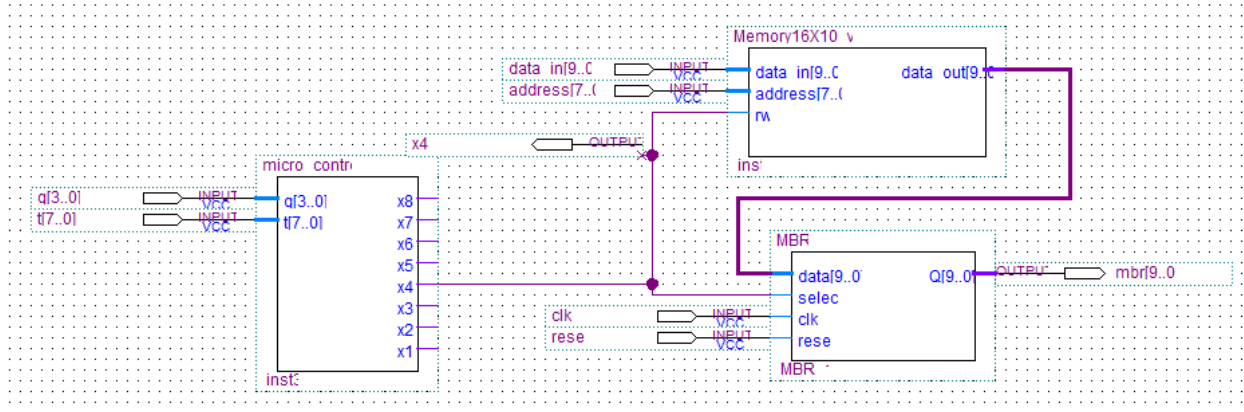


Figure 33:X4 test

 


Figure 34:x4 wave

When x4 is one the data in the memory will be transfer from memory to the mbr for example at address 4 the data will be 1000001101 and that what the mbr takes and x4 will be on when the address is 4

X8

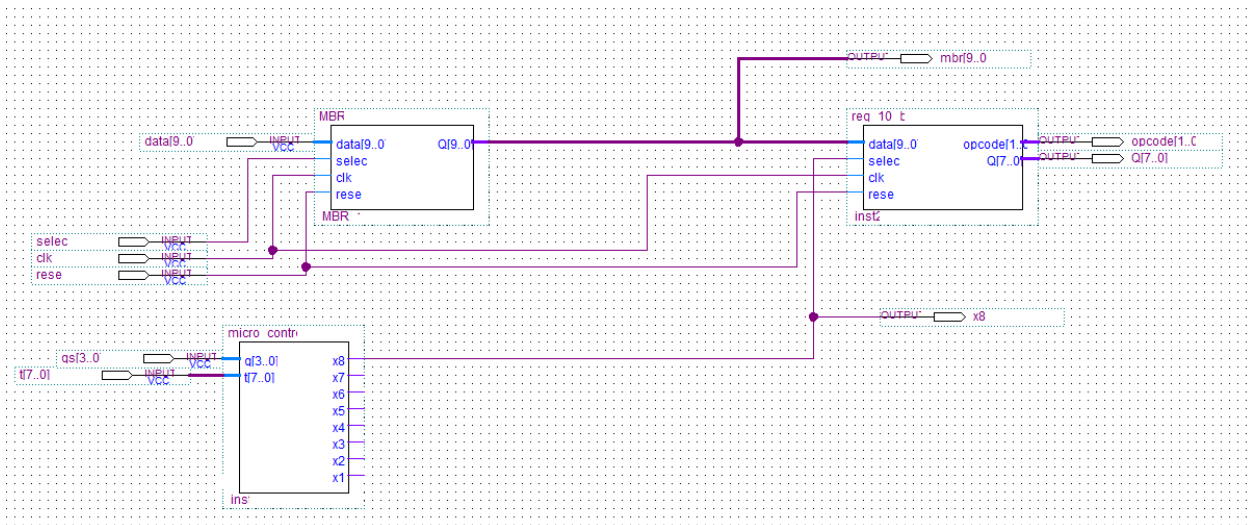


Figure 35:X8 tets

 


Figure 36:x8 wav

# microcomputer

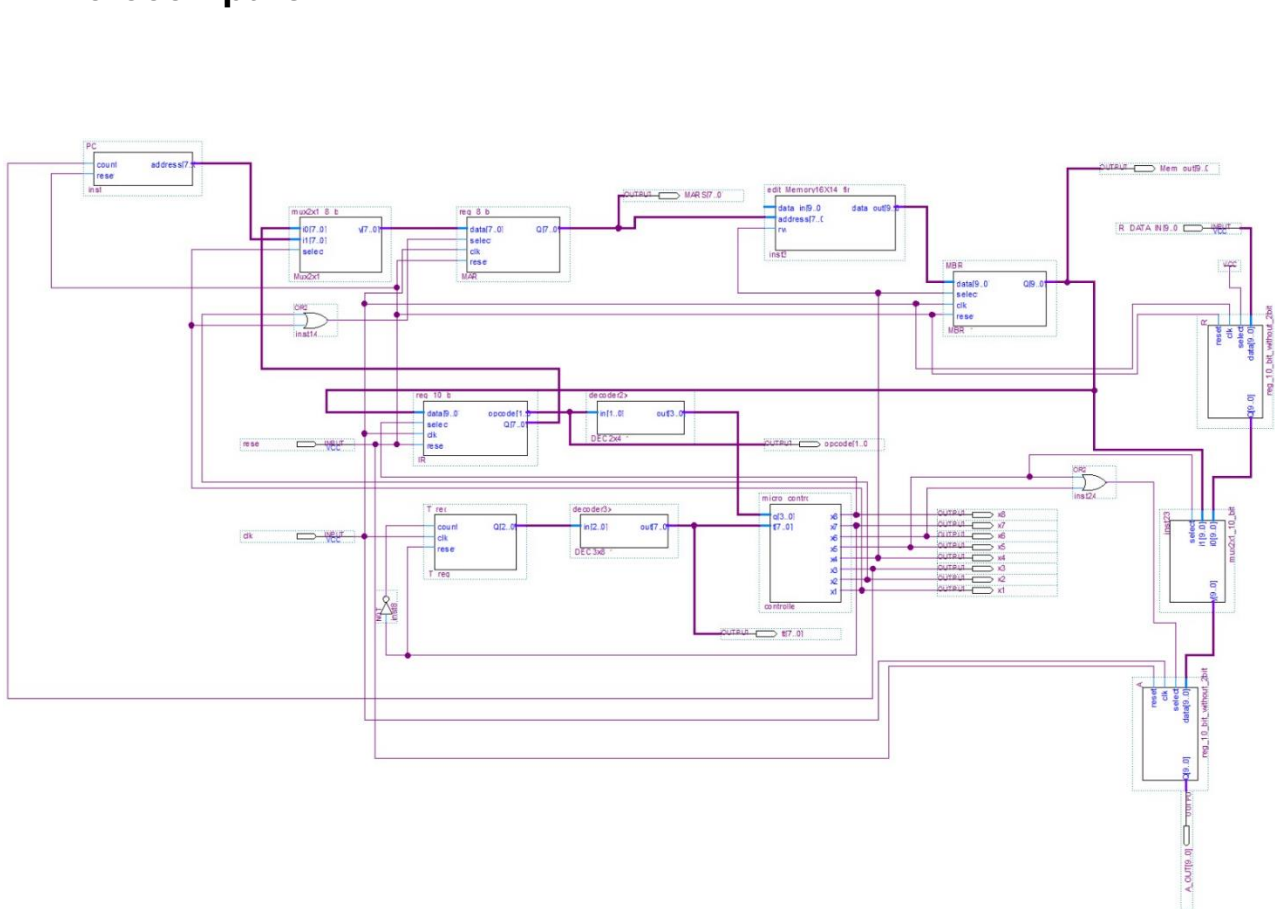


Figure 37: microcomputer block diagram

 


Figure 38: microcomputer block diagram waveform

When the opcode be (00) there is no sequence to do when it is (01) transfer the data from R to A

When it is (10) transfer the data in the MBR to A when it is (11) transfer the data from memory to A

01: after T finishes 3 clocks the instruction will be in R( 0110111100) but A will take the first 8 bit from R because in 10 operation it required the operand so A should be 8 bit register but I made it 10 bit register and it will take but the last two bit 00 so A (0010111100)

10: after T finishes 5 clocks the instruction will be 11000011100 the operand of this instruction 0111100 so A 000111100

11 after T finish 7 clock the instruction will be 0000001100 will be in A

## Question two

### arithmetic circuit

```

1 module arthimtic_circuit (output [7:0]D,output cout , input [7:0]A,B ,input cin, input [1:0]S);
2 wire c1,c2,c3 ,c4,c5,c6,c7;
3 wire y0,y1,y2,y3 ,y4,y5,y6,y7;
4 |
5 mux4x1 mx0 (y0,B[0],~B[0],1'b0,1'b1,S[0],S[1]),
6       mx1 (y1,B[1],~B[1],1'b0,1'b1,S[0],S[1]),
7       mx2 (y2,B[2],~B[2],1'b0,1'b1,S[0],S[1]),
8       mx3 (y3,B[3],~B[3],1'b0,1'b1,S[0],S[1]),
9       mx4 (y4,B[4],~B[4],1'b0,1'b1,S[0],S[1]),
10      mx5 (y5,B[5],~B[5],1'b0,1'b1,S[0],S[1]),
11      mx6 (y6,B[6],~B[6],1'b0,1'b1,S[0],S[1]),
12      mx7 (y7,B[7],~B[7],1'b0,1'b1,S[0],S[1]);
13
14 full_adder FA0 (D[0],c1,A[0],y0,cin),
15             FA1 (D[1],c2,A[1],y1,c1),
16             FA2 (D[2],c3,A[2],y2,c2),
17             FA3 (D[3],c4,A[3],y3,c3),
18             FA4 (D[4],c5,A[4],y4,c4),
19             FA5 (D[5],c6,A[5],y5,c5),
20             FA6 (D[6],c7,A[6],y6,c6),
21             FA7 (D[7],cout,A[7],y7,c7);
22
23 endmodule

```

Figure 39:arithmetiv circuit cod

 


Figure 40:arithmetic circuit waveform

Select			Input Y	Output		Microoperation
S <sub>1</sub>	S <sub>0</sub>	C <sub>in</sub>		D = A + Y + C <sub>in</sub>		
0	0	0	B	D = A + B		Add
0	0	1	B	D = A + B + 1		Add with carry
0	1	0	$\overline{B}$	D = A + $\overline{B}$		Subtract with borrow
0	1	1	$\overline{B}$	D = A + $\overline{B}$ + 1		Subtract
1	0	0	0	D = A		Transfer A
1	0	1	0	D = A + 1		Increment A
1	1	0	1	D = A - 1		Decrement A
1	1	1	1	D = A		Transfer A

Figure 41;arithmetic circuit Truth table

## Logic circuit

```

1 module logic_circuit (output [7:0]E , input[7:0]A,B ,input [1:0]S);
2
3 wire [7:0] and_op,or_op,xor_op,not_op ;
4 // 00 -> A and B , 01 -> A or B , 10 -> A xor B , 11 -> not A
5 assign and_op = A & B ;
6 assign or_op = A | B ;
7 assign xor_op = A ^ B ;
8 assign not_op = ~A ;
9
10 mux4x1 mx0(E[0],and_op[0],or_op[0],xor_op[0],not_op[0],S[0],S[1]),
11 mx1(E[1],and_op[1],or_op[1],xor_op[1],not_op[1],S[0],S[1]),
12 mx2(E[2],and_op[2],or_op[2],xor_op[2],not_op[2],S[0],S[1]),
13 mx3(E[3],and_op[3],or_op[3],xor_op[3],not_op[3],S[0],S[1]),
14 mx4(E[4],and_op[4],or_op[4],xor_op[4],not_op[4],S[0],S[1]),
15 mx5(E[5],and_op[5],or_op[5],xor_op[5],not_op[5],S[0],S[1]),
16 mx6(E[6],and_op[6],or_op[6],xor_op[6],not_op[6],S[0],S[1]),
17 mx7(E[7],and_op[7],or_op[7],xor_op[7],not_op[7],S[0],S[1]);
18
19
20 endmodule

```

Figure 42:Logic circuit cod

 


Figure 43:logic circuit waveform

Select			Input Y	Output		Microoperation
S <sub>1</sub>	S <sub>0</sub>	C <sub>in</sub>		D = A + Y + C <sub>in</sub>		
0	0	0	B	D = A + B		Add
0	0	1	B	D = A + B + 1		Add with carry
0	1	0	$\overline{B}$	D = A + $\overline{B}$		Subtract with borrow
0	1	1	$\overline{B}$	D = A + $\overline{B}$ + 1		Subtract
1	0	0	0	D = A		Transfer A
1	0	1	0	D = A + 1		Increment A
1	1	0	1	D = A - 1		Decrement A
1	1	1	1	D = A		Transfer A

Figure 44:logic circuit Truth table

# ALU

```

1 module ALU (output [7:0] F ,output cout , input [7:0] A,B, input cin , S2,S1,s0);
2
3 wire [7:0] logic ,arithmtic ;
4
5
6 arthimtic_circuit(arthimtic,cout,A,B,cin,{S1,S0});
7 logic_circuit(logic,A,B,{S1,S0});
8 mux2x1_8_bit main_mx(F,arthimtic,logic,S2);
9
10 endmodule

```

Figure 45:ALU code

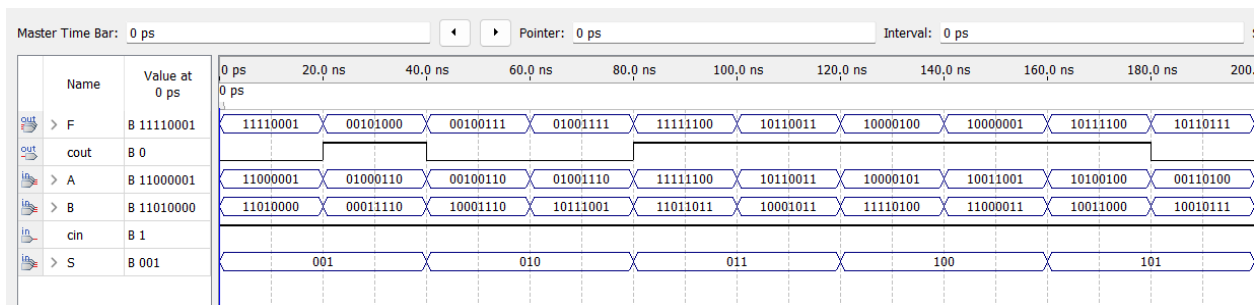


Figure 46:ALU wave

## state controller

```

1  module state_controller(output [7:0]y,input S,E,qa,qs,clk,reset) ;
2  reg [7:0] state ;
3  parameter T0=8'b00000001,
4             T1=8'b00000010,
5             T2=8'b00000100,
6             T3=8'b00001000,
7             T4=8'b00010000,
8             T5=8'b00100000,
9             T6=8'b01000000,
10            T7=8'b10000000;
11  always@(posedge clk )
12  begin
13      if (reset==1) state <= T0 ;
14      else case(state)
15
16          T0:  if(qs==1) state <= T1 ;else if (qa==1) state<= T2 ; else state <= T0 ; // if qs ==1 state will become T1 else remain the same
17          T1:  state <= T2 ;
18          T2:  if(S==1) state <= T4 ; else state <= T3 ;
19          T3:  state <= T0 ;
20          T4:  state<= T5 ;
21          T5:  if (E==0) state<= T6 ; else state <= T0 ;
22          T6:  state <= T7 ;
23          T7:  state <= T0;
24      endcase
25  end
26  assign y = state ;

```

Figure 48:state\_controller

 


Figure 47:state control waveform

**HDL Example 5.6 (Moore Machine: Zero Detector)**

```

// Moore model FSM (see Fig. 5.19)
module Moore_Model_Fig_5_19 (
    output [1: 0] y_out,
    input x_in, clock, reset
);
    reg [1: 0] state;
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
    always @(posedge clock, negedge reset)
        if (reset == 0) state <= S0; // Initialize to state S0
        else case (state)
            S0: if (~x_in) state <= S1; else state <= S0;
            S1: if (x_in) state <= S2; else state <= S3;
            S2: if (~x_in) state <= S3; else state <= S2;
            S3: if (~x_in) state <= S0; else state <= S3;
        endcase
    assign y_out = state; // Output of flip-flops
endmodule

```

Figure 49:Moore machine code



## Hardware state

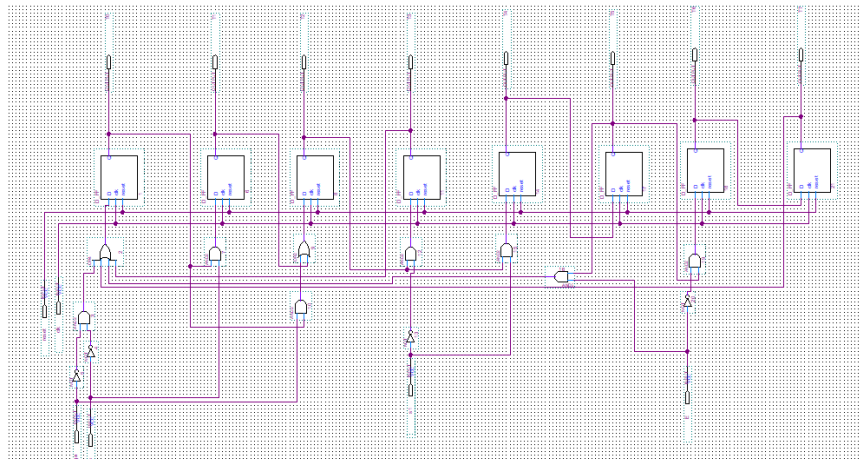


Figure 50:hardware state

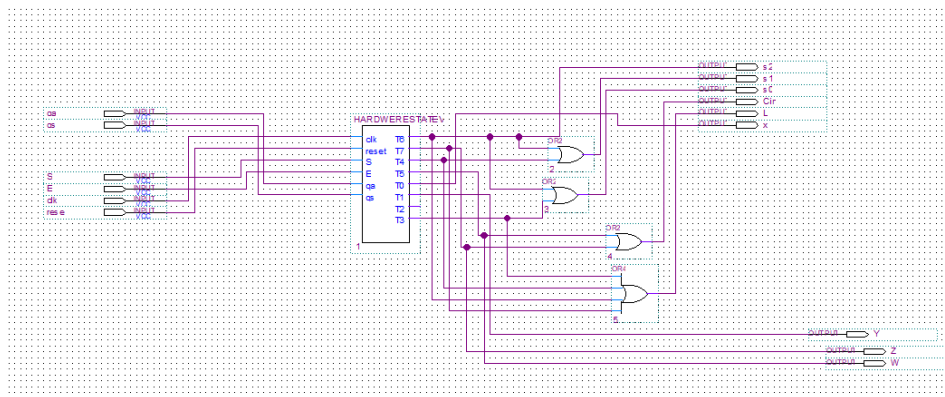


Figure 51 state with output

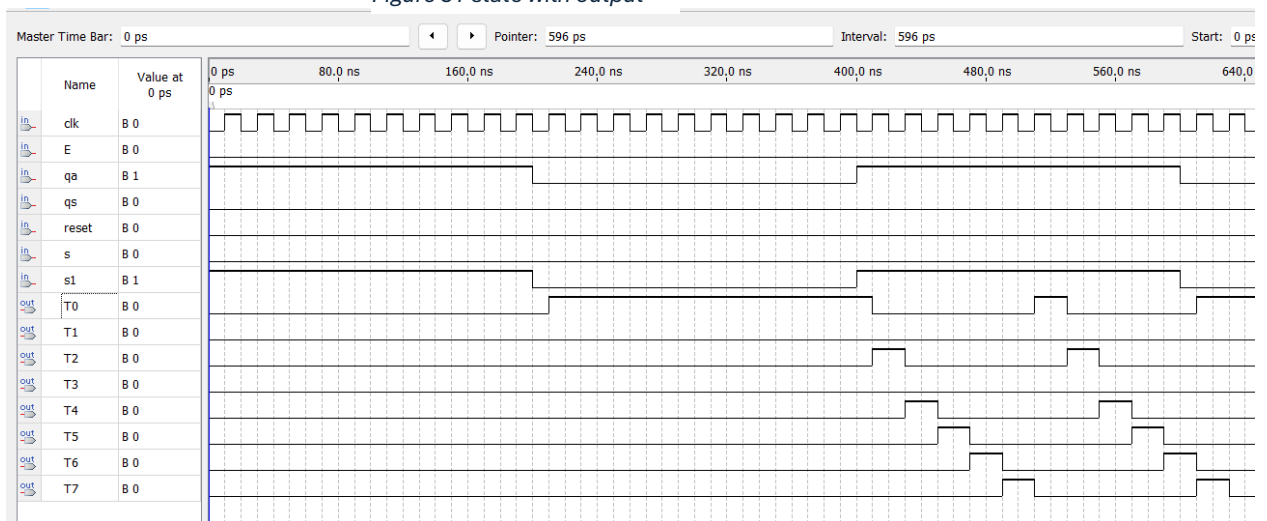


Figure 52hardware state wave

# ALU with state controller

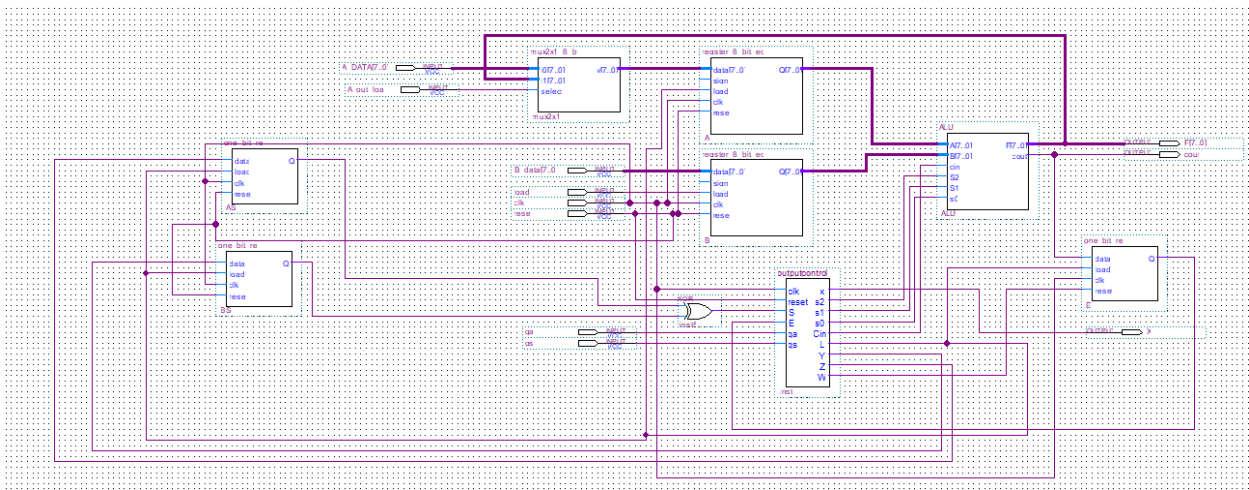


Figure 53:ALU with state control block

 


Figure 54 alu with state wave form

## ROM8X14

```

1  module ROM8x14t(output reg X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0,input [2:0] data_in );
2  always @(data_in)
3
4  case(data_in)
5
6      3'b000: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} =14'b10000000000001;
7      3'b001: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b000000010001001;
8      3'b010: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b00000000010010;
9      3'b011: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b00010100000001;
10     3'b100: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b00101100010101;
11     3'b101: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b10000000100011;
12     3'b110: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b01110100011101;
13     3'b111: {X,S2,S1,S0,Cin,L,Y,Z,W,A2,A1,A0,MUX_s1,MUX_s0} = 14'b00001101000000;
14
15     endcase
16
17 endmodule

```

Figure 55:ROM8X14 code

 


Figure 56:ROM8X14 waveform

# CAR

```
1 module CARt(output reg [2:0] adres,input d1,d2,d3,load,increment);
2 always @(*)
3 begin
4   if(load)
5   begin
6     adres[0]=d1;
7     adres[1]=d2;
8     adres[2]=d3;
9   end
10  else
11  begin
12    adres[0]=d1+1'b0;
13    adres[1]=d2+1'b1;
14    adres[2]=d3+1'b1;
15  end
16 end
17 endmodule
18 |
```

Figure 57:CAR code

## Hardware control

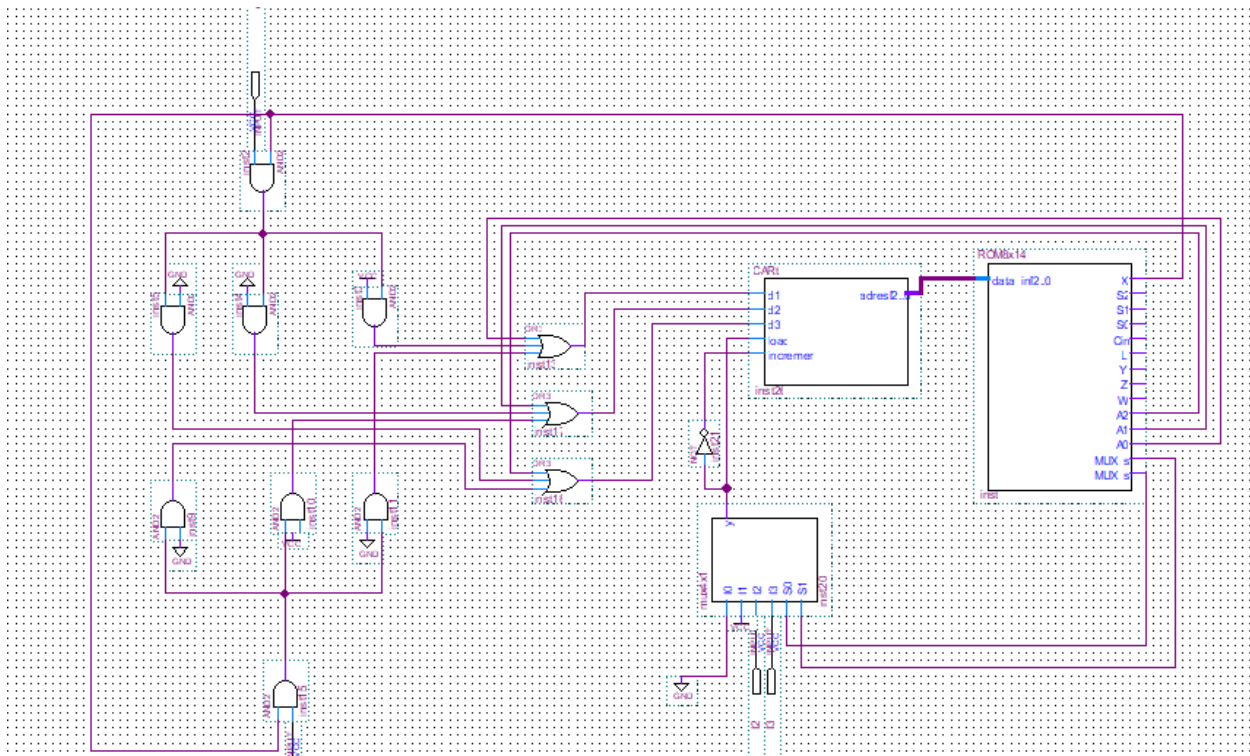


Figure 58:hardwire control implmen

# Hardwar control with ALU

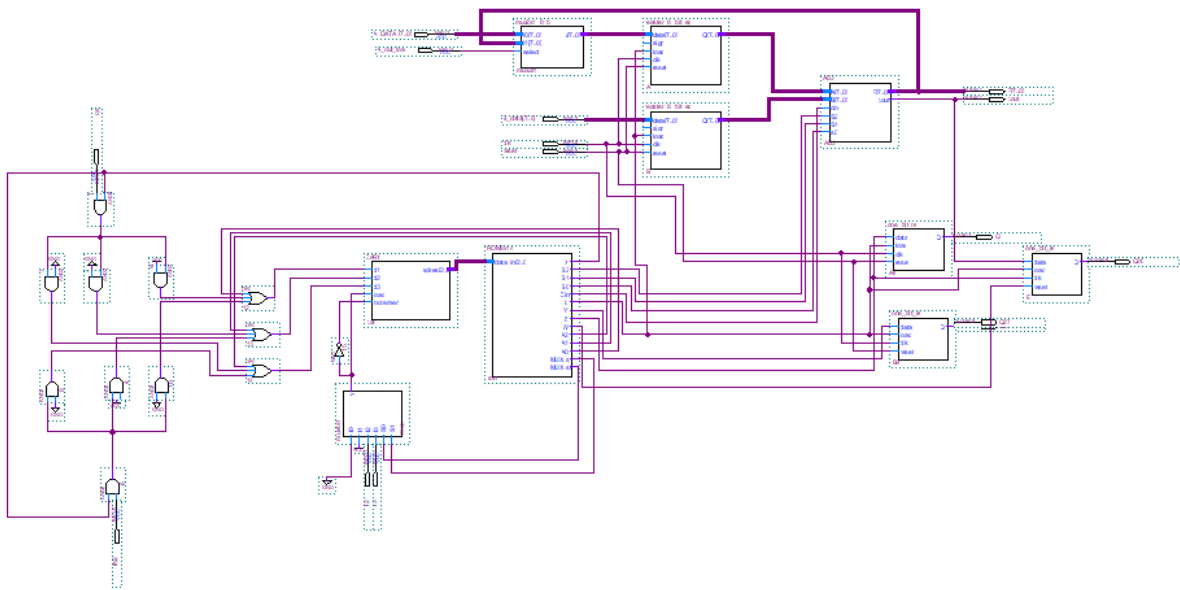


Figure 60:hardware control with alu

 


Figure 59:Question2 output

Blocks digrams

 


Figure 63:control unit

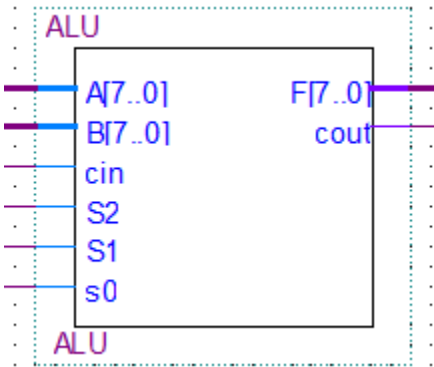


Figure 62:ALU

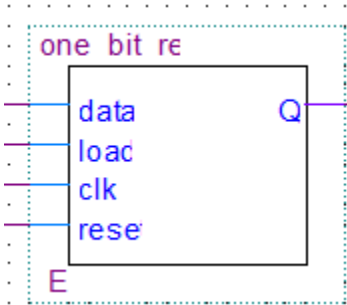


Figure 61:E

 


Figure 64:A&B

## COMMON use circuit

```

1 module mux2x1(output out ,
2               input i0,i1,
3               input s);
4
5   assign out = (s) ? i1:i0 ;
6
7   endmodule
8

```

Figure 65:Mux2x1

 


Figure 66MUX2X1 block

```

1 module decoder2x4(input[1:0] in,output reg[3:0] out);
2
3   initial out = 4'b0000;
4   always @(in )
5   begin
6
7     case (in)
8     2'b00: out=4'b0001;
9     2'b01: out=4'b0010;
10    2'b10: out=4'b0100;
11    2'b11: out=4'b1000;
12  endcase
13  end
14
15 endmodule

```

 


Figure 67:Decode 2X4 block

Figure 68:decoder 2x4

```

1 module mux4x1(output y ,input I0,I1,I2,I3, input S0,S1 );
2
3 wire y0,y1,y2,y3 ;
4 and a0(y0,I0,~S0,~S1),
5     a1(y1,I1,S0,~S1),
6     a2(y2,I2,~S0,S1),
7     a3(y3,I3,S0,S1);
8 or o1(y,y0,y1,y2,y3);
9
10
11
12
13 endmodule

```

Figure 69:MUX4x1

```

1 Smodule D_FF (output reg Q , input D,clk,reset ) ;
2
3 always @(posedge clk )
4 begin
5     if(reset == 1)
6         Q <= 1'b0 ;
7     else
8         Q <= D ;
9
10 end
11
12
13
14 endmodule

```

Figure 70:Dflipflop

```

1 module decoder3x8structure (output [7:0]t_out,input[2:0] tin );
2 wire n1,n2,n3;
3 not a(n1,tin[0]);
4 not b(n2,tin[1]);
5 not c(n3,tin[2]);
6
7 and (t_out[0], n1, n2, n3); // 000
8 and (t_out[1], tin[0], n2, n3); // 001
9 and (t_out[2], n1, tin[1], n3); // 010
10 and (t_out[3], tin[0], tin[1], n3); // 011
11 and (t_out[4], n1, n2, tin[2]); // 100
12 and (t_out[5], tin[0], n2, tin[2]); // 101
13 and (t_out[6], n1, tin[1], tin[2]); // 110
14 and (t_out[7], tin[0], tin[1], tin[2]); // 111
15
16 endmodule

```

 


Figure 71:Decoder3x8 BLOCK



Figure 72:Decoder 3X8

```
1  module T_FF(output reg Q ,input T,clk,reset);
2
3
4  always@(posedge clk )
5  begin
6      if(reset == 1)
7      begin
8          Q <= 1'b0 ;
9      end
10     else
11     begin
12         Q <= Q ^ T ;
13     end
14 end
15
16 //assign nQ = ~Q;
17
18 endmodule
```

Figure 73:Tflipflop